

Yihui Wang

October 11, 2022

ECE 6240

### Lab#7 Dynamic Circuits using Domino Logic

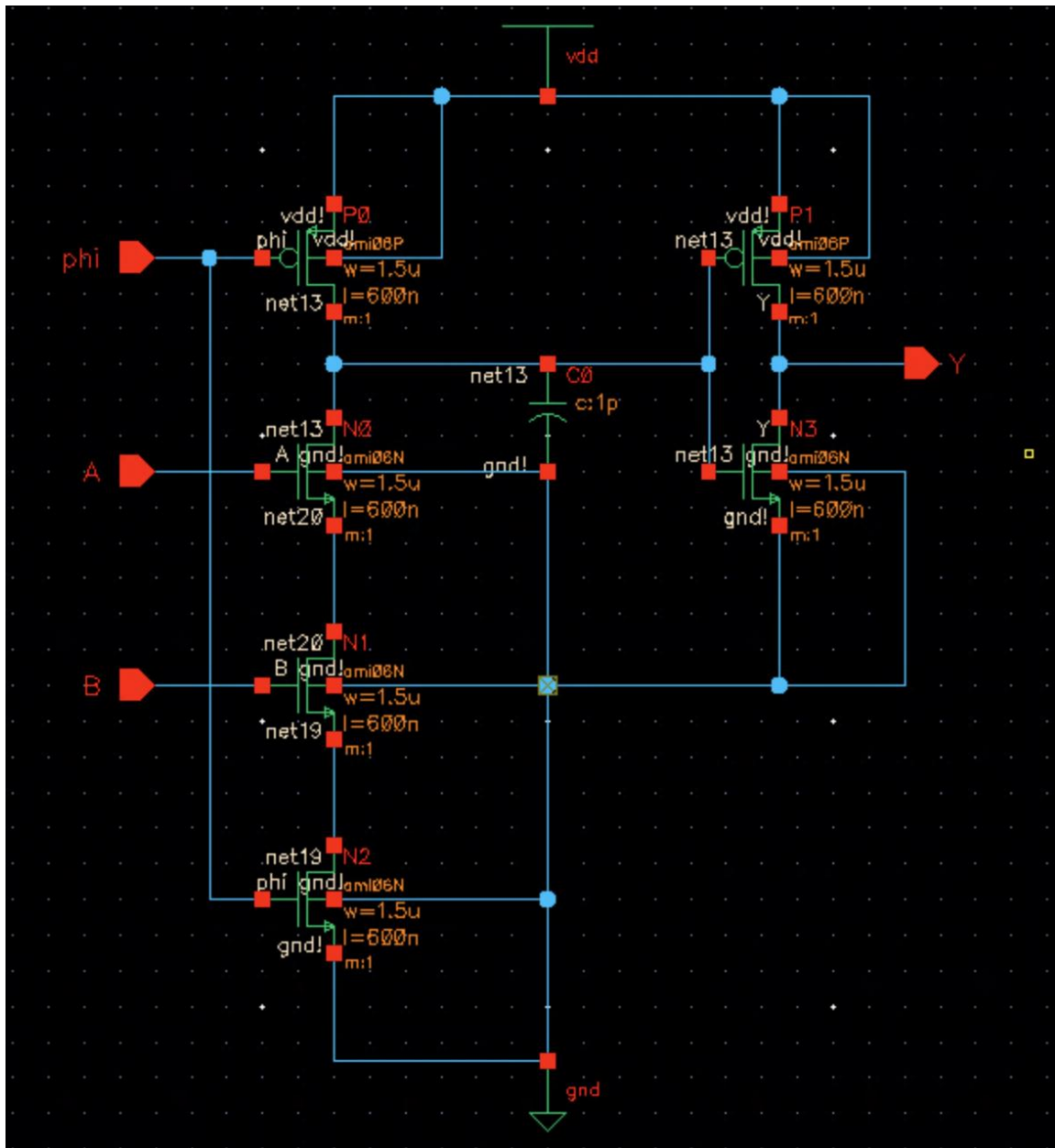


Figure 1 Schematic

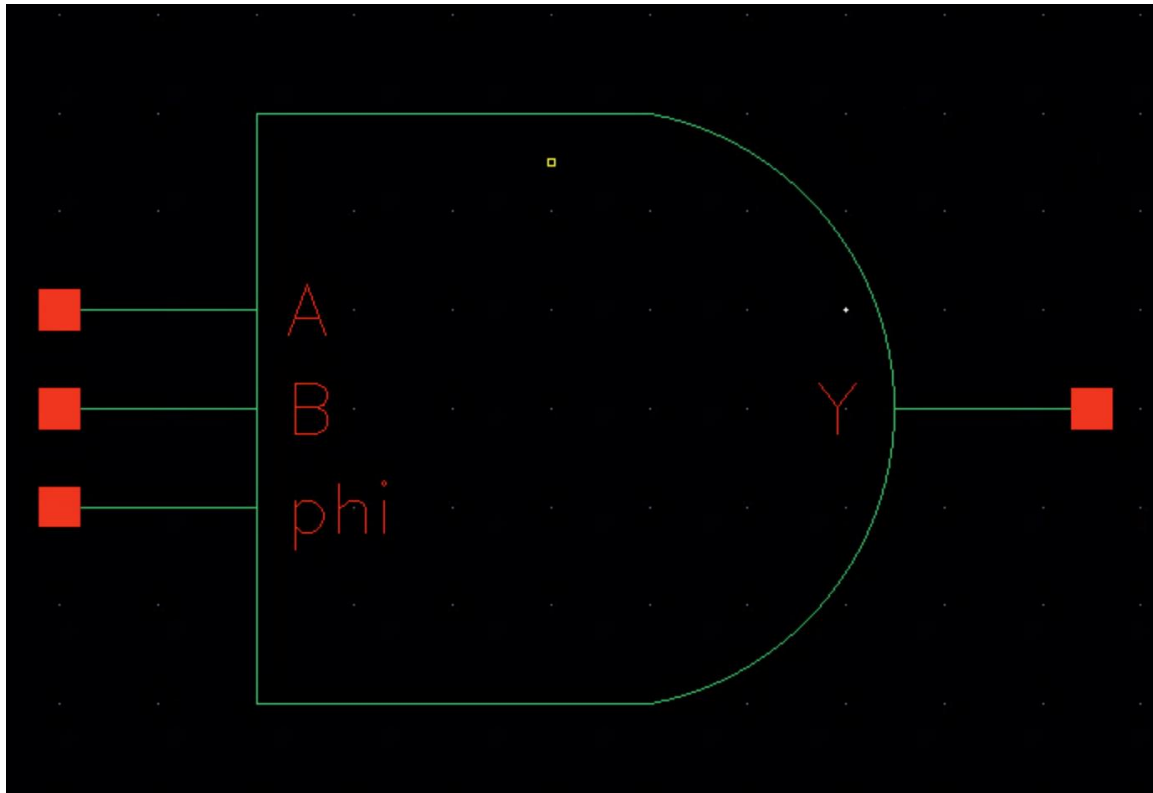


Figure 2 Symbol

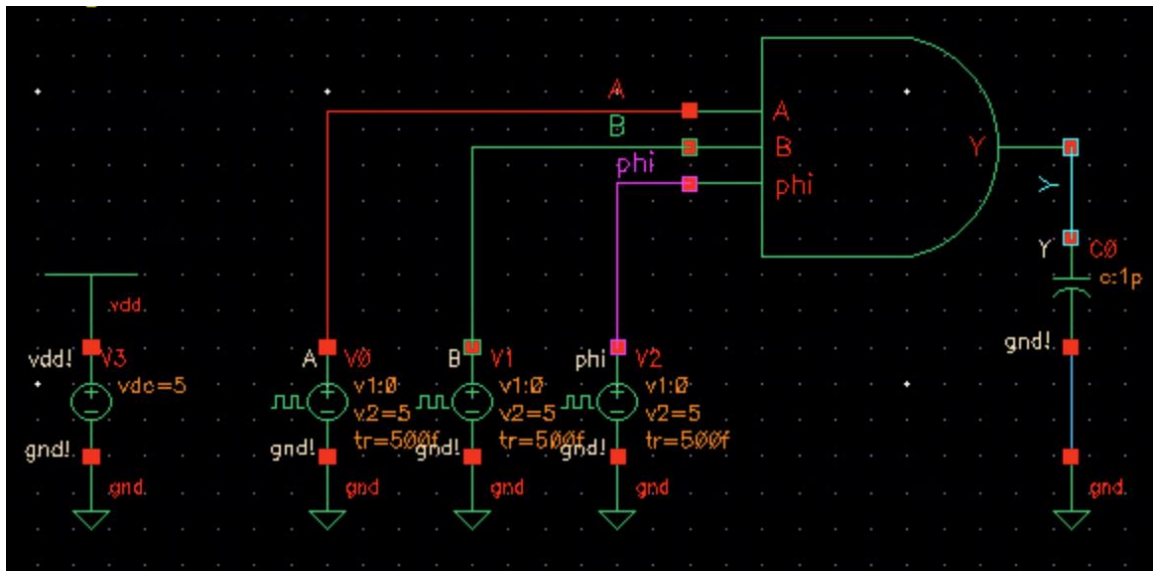


Figure 3 Testbench Schematic

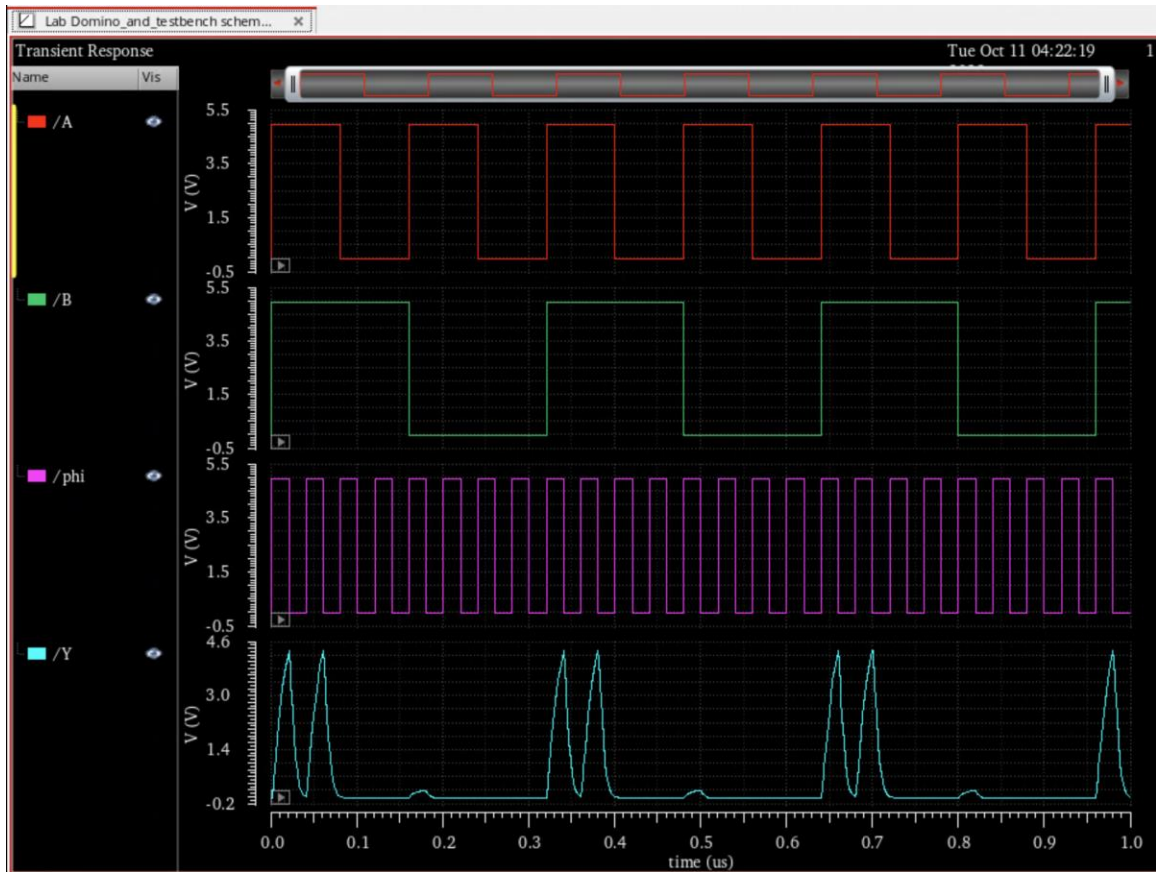


Figure 4 Testbench Result

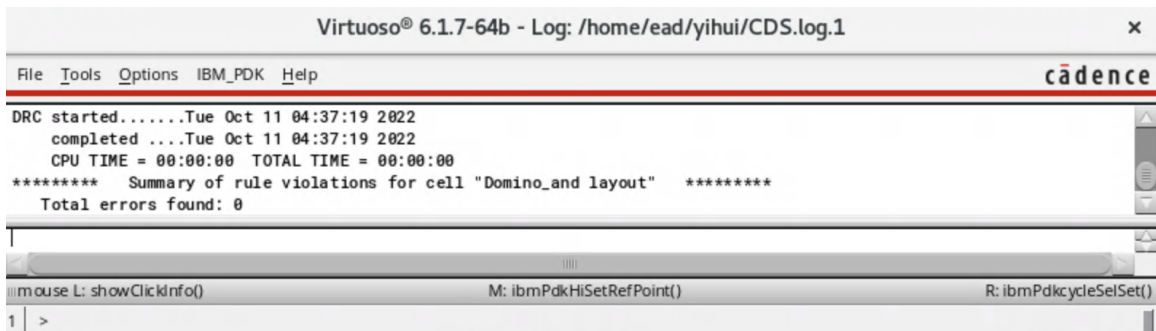


Figure 5 DRC Result

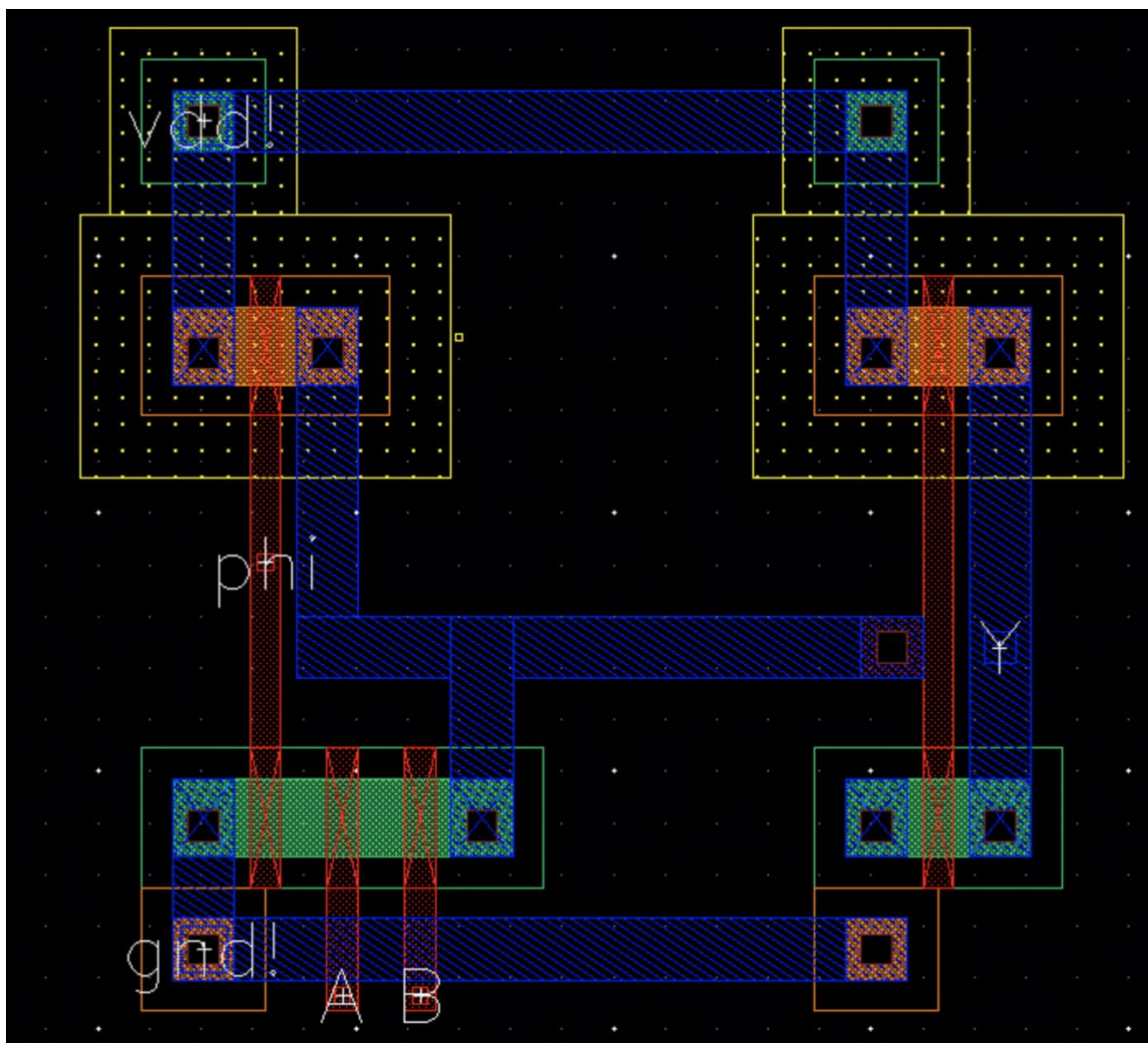


Figure 6 Layout

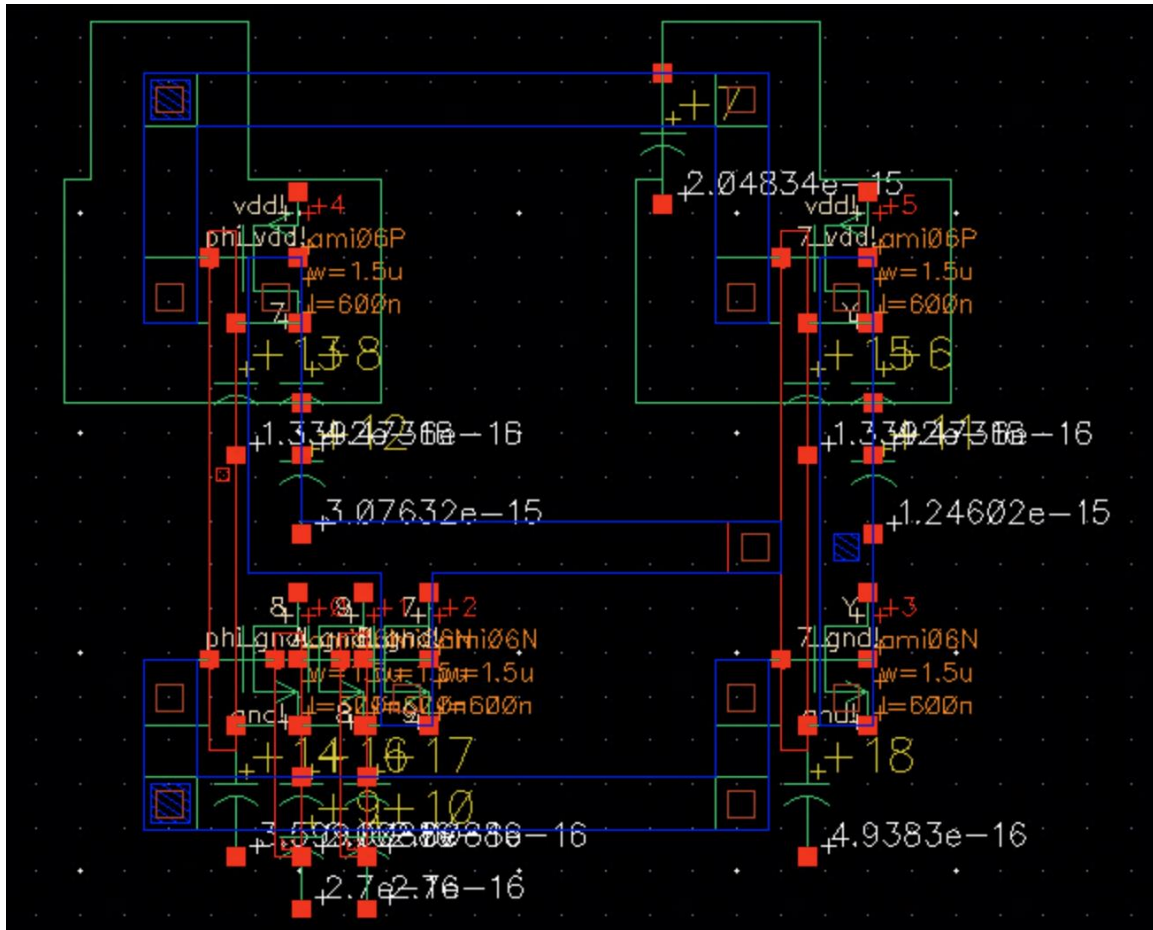


Figure 7 Extracted Layout

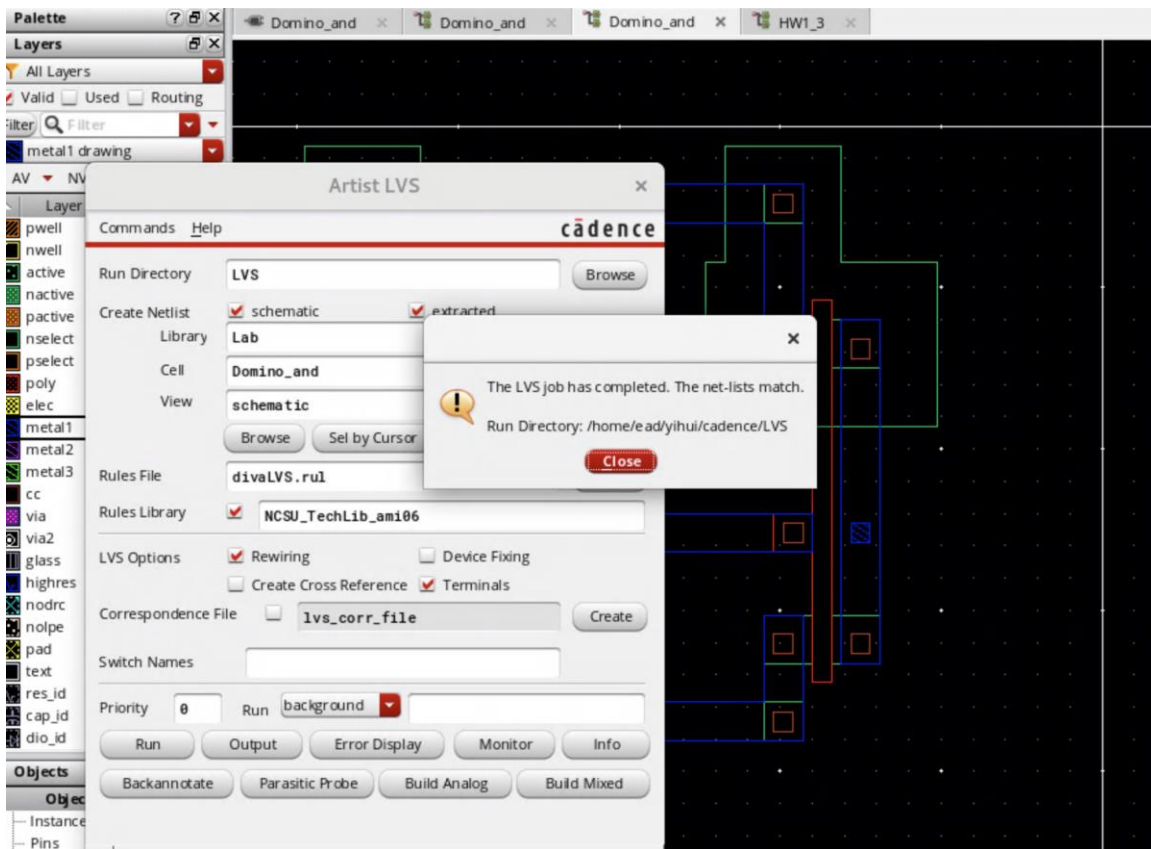


Figure 8 LVS Result

For static AND gate:  $18 \times 22.35 = 402.3 \mu\text{m}^2$ , for domino AND gate:  $20.25 \times 19.05 = 385.76 \mu\text{m}^2$