

Yihui Wang

September 19, 2022

ECE 6240

Lab#2 Transient and DC w/ Parametric Analysis

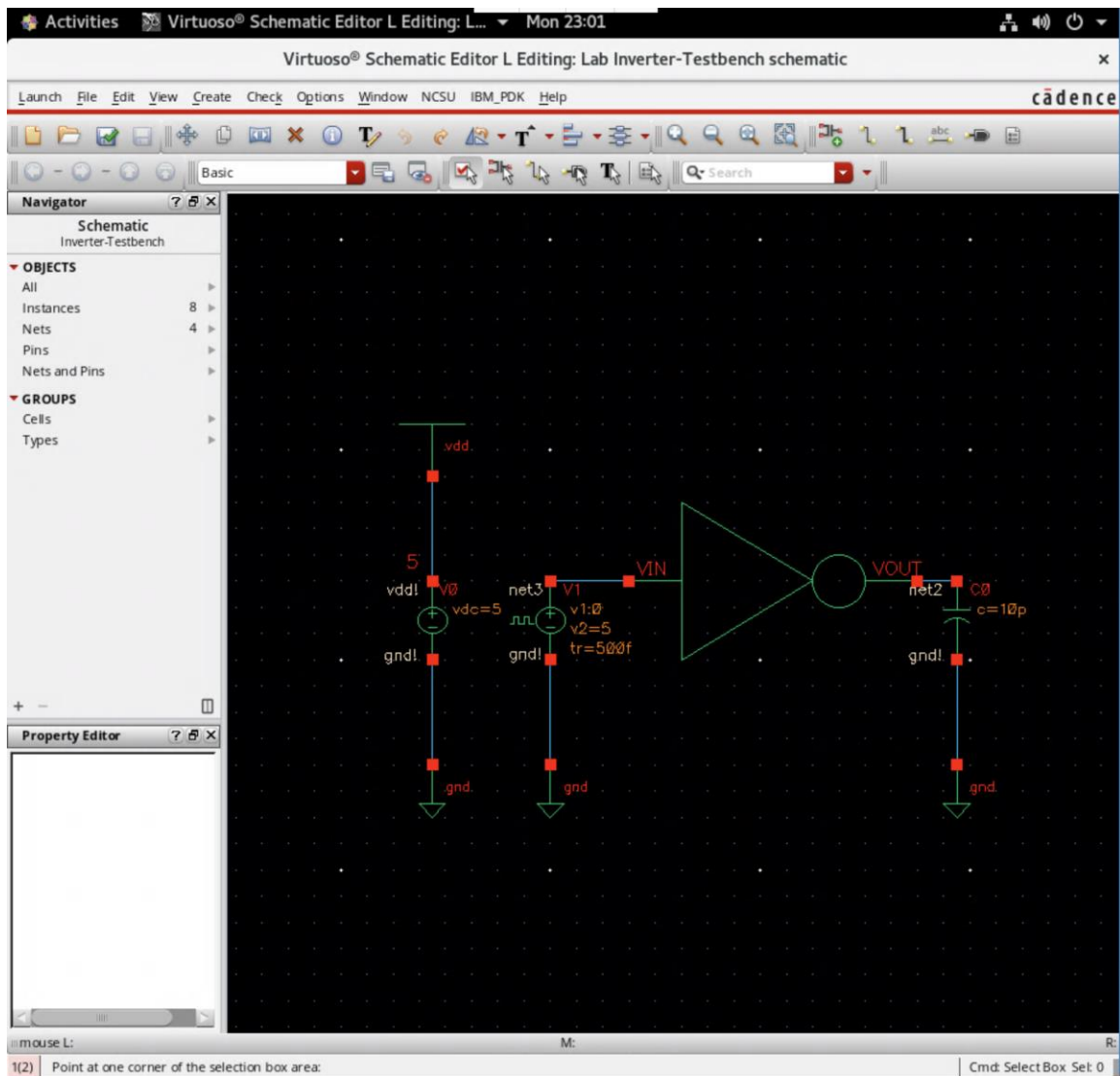


Figure 1 Testbench Schematic

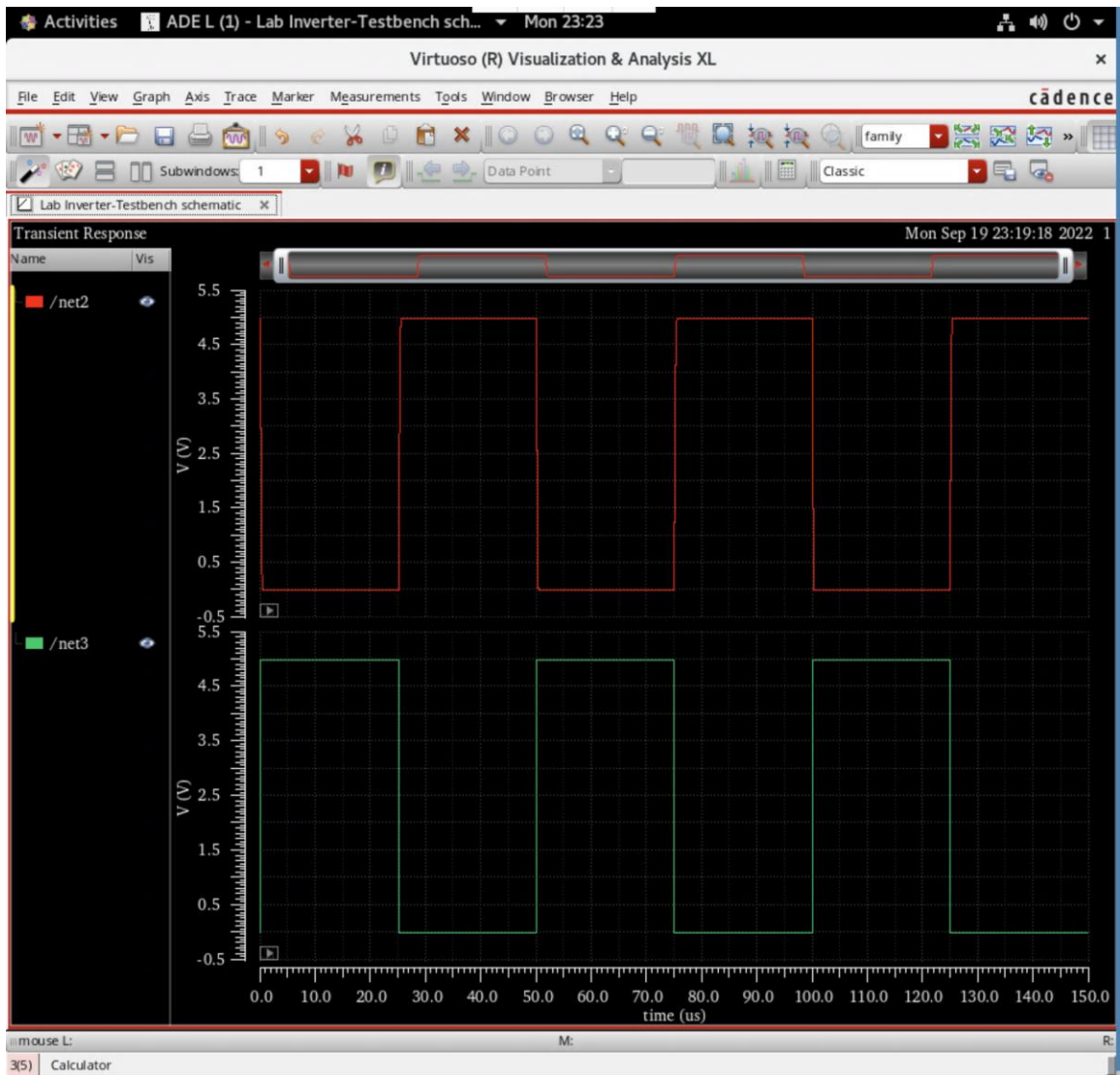


Figure 2 Transient Analysis

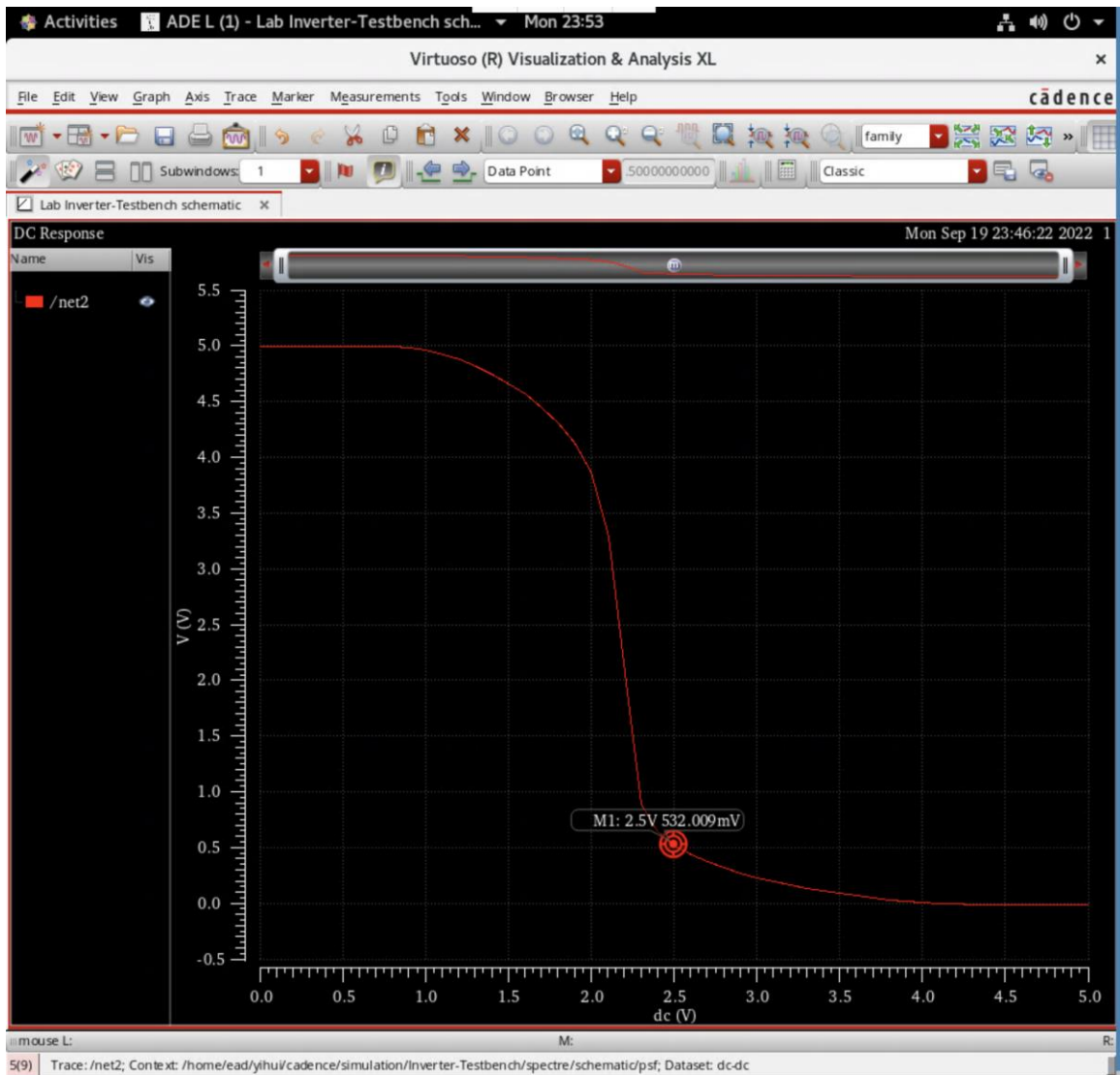


Figure 3 DC Analysis

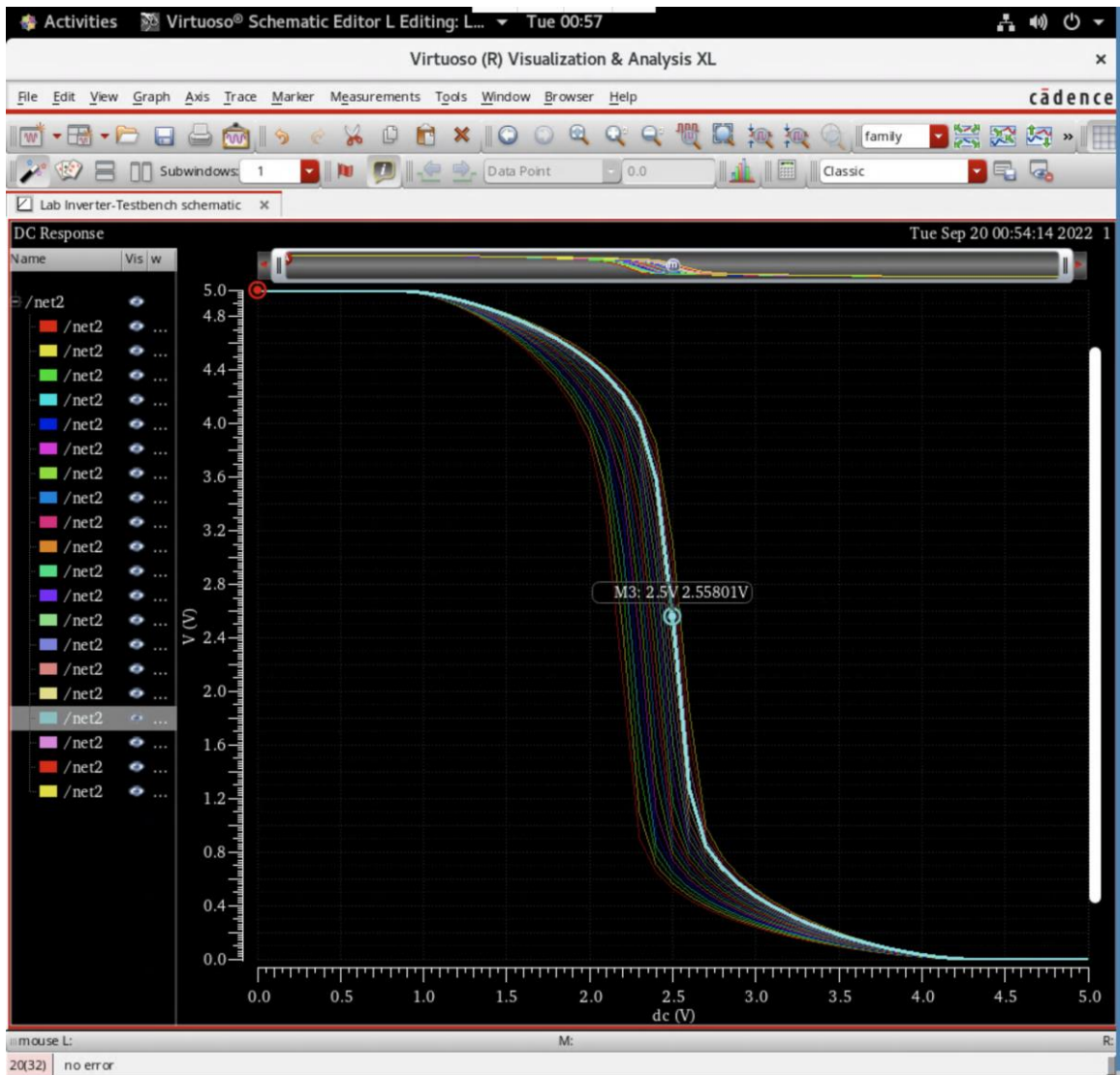


Figure 4 Parametric Analysis (20 steps)

The best width is 2.342105u.